

# Inf2C - Computer Systems

## Lecture 9

### Processor Design – Single Cycle

---

Boris Grot

School of Informatics  
University of Edinburgh




# Previous lectures

---

- Combinational circuits
  - Combinations of gates (INV, AND, OR, NOR..)
  - Output: function of the input only (memory-less)
- Sequential circuits
  - Output: function of the input and prev inputs
  - Basic memory element: SR-latch (cross-coupled NORs)
  - Clock: synchronizes the operation of the circuit
  - Operation: current states + inputs go through combinational logic. Next states stored in a register on a rising clock edge.
- Hardware Finite State Machines (FSMs)
  - Registers for states + comb'l logic for transitions & outputs
 
# Lecture 9: Processor design – single cycle

- Motivation:
  - Learn how to design a simple processor
- Two main parts:
  - Datapath: performs the data operations as commanded by the program instructions
  - Control: controls the datapath, memory and I/O according to the program instructions
- Using:
  - Combinational and sequential circuits described in previous lectures



# Design steps / Lecture outline

---


- Step 1: Determine the components required by understanding main processor functions
- Step 2: Build the datapath
- Step 3: Build the control
  
- Show the execution of a few instructions on the designed machine

# Main processor functions

---


- **Fetch** instruction from instruction memory
- Read the register operands
- Use the ALU for computation
  - Arithmetic, memory address, branch target address
- Access data memory for load/store
- Store the result of computation or loaded data into the destination register
- Update the Program Counter (PC)

# Instruction Fetch

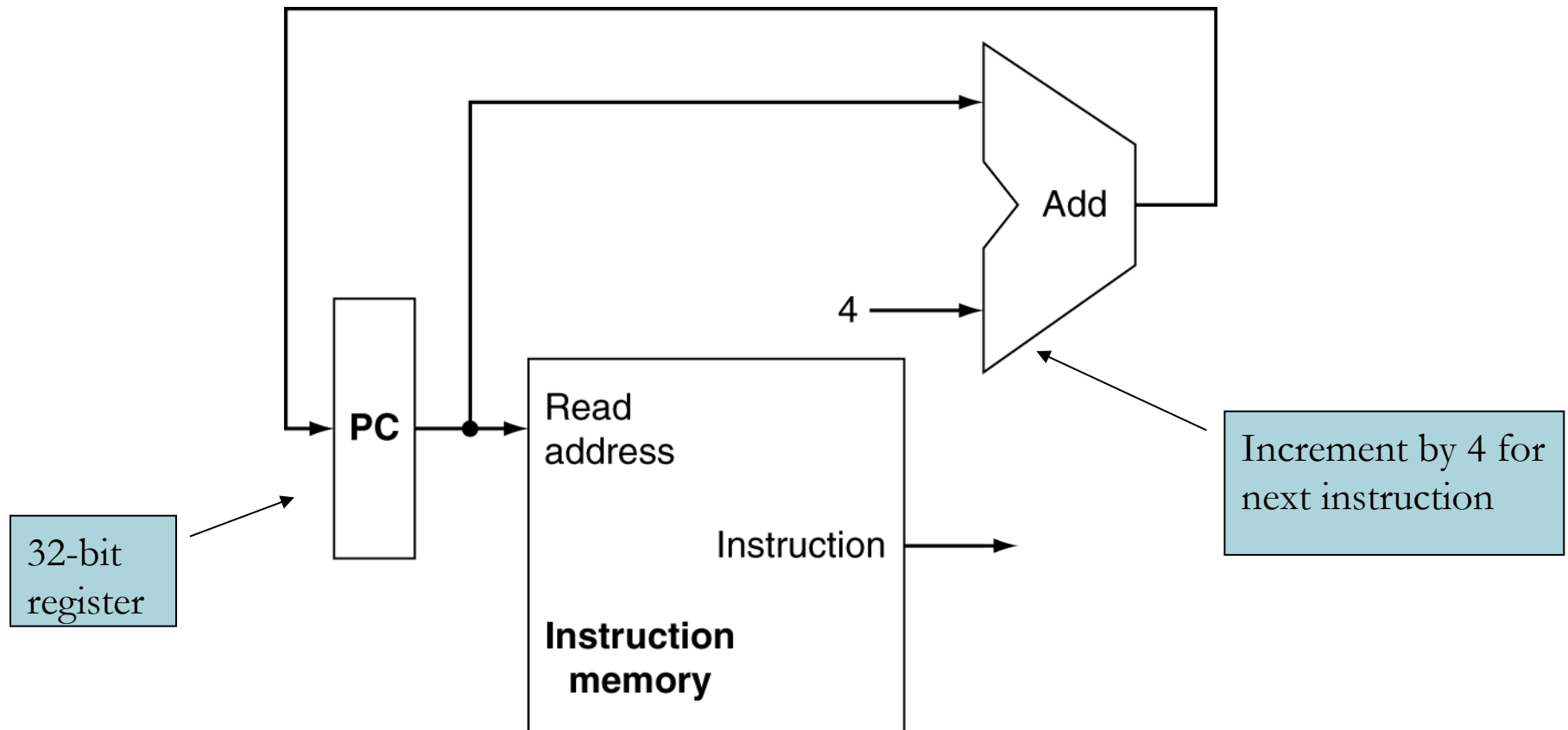

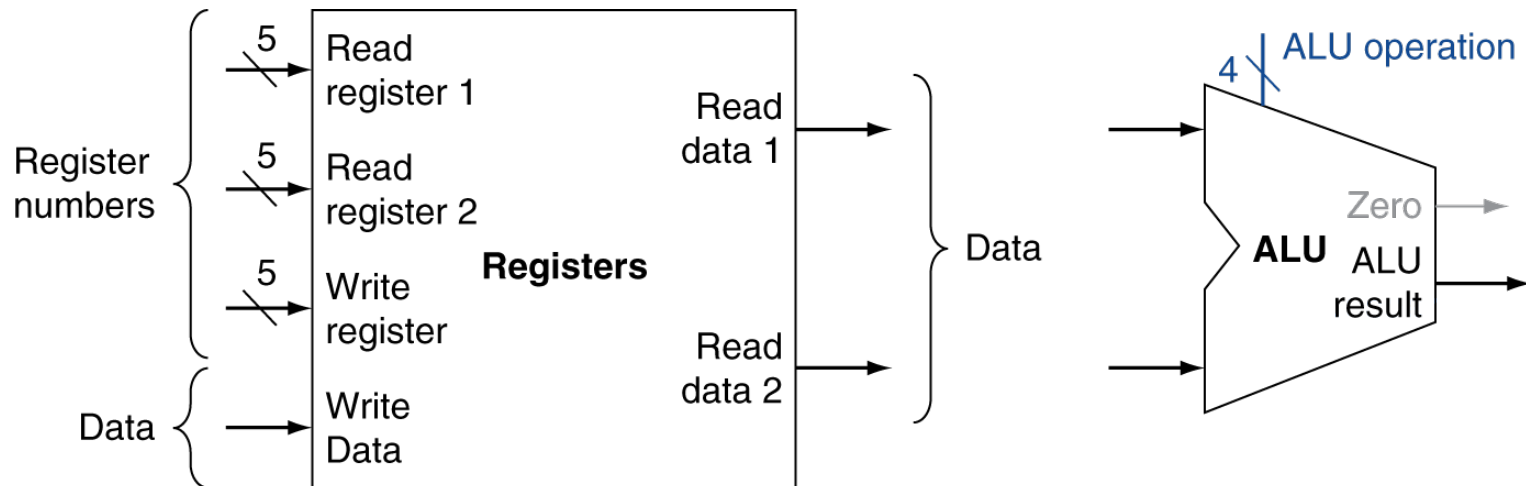
# R-Format Instructions

- Read two register operands
- Perform arithmetic/logical operation
- Write register result


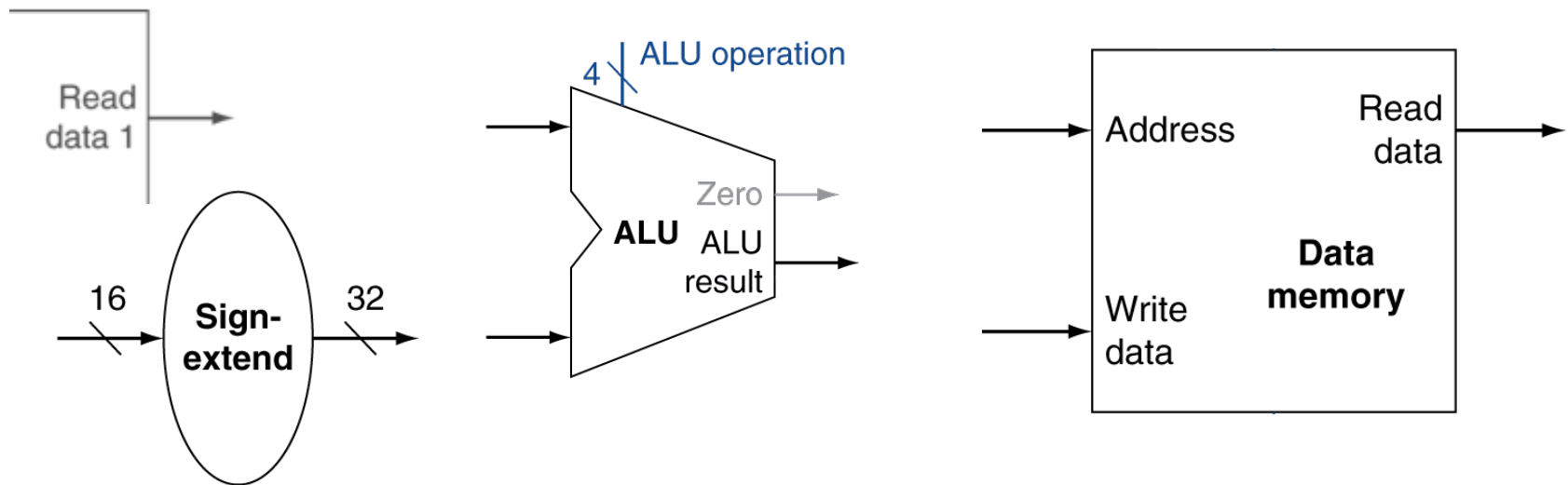
# Load/Store Instructions

- Read register operands
- Calculate address using 16-bit offset
  - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory






# Branch Instructions


---

- Read register operands
- Compare operands
  - Use ALU, subtract and check Zero output
- Calculate target address
  - Sign-extend the immediate (offset)
  - Shift left 2 places (word align)
  - Add to PC + 4
    - Already calculated by instruction fetch


# Branch Instructions

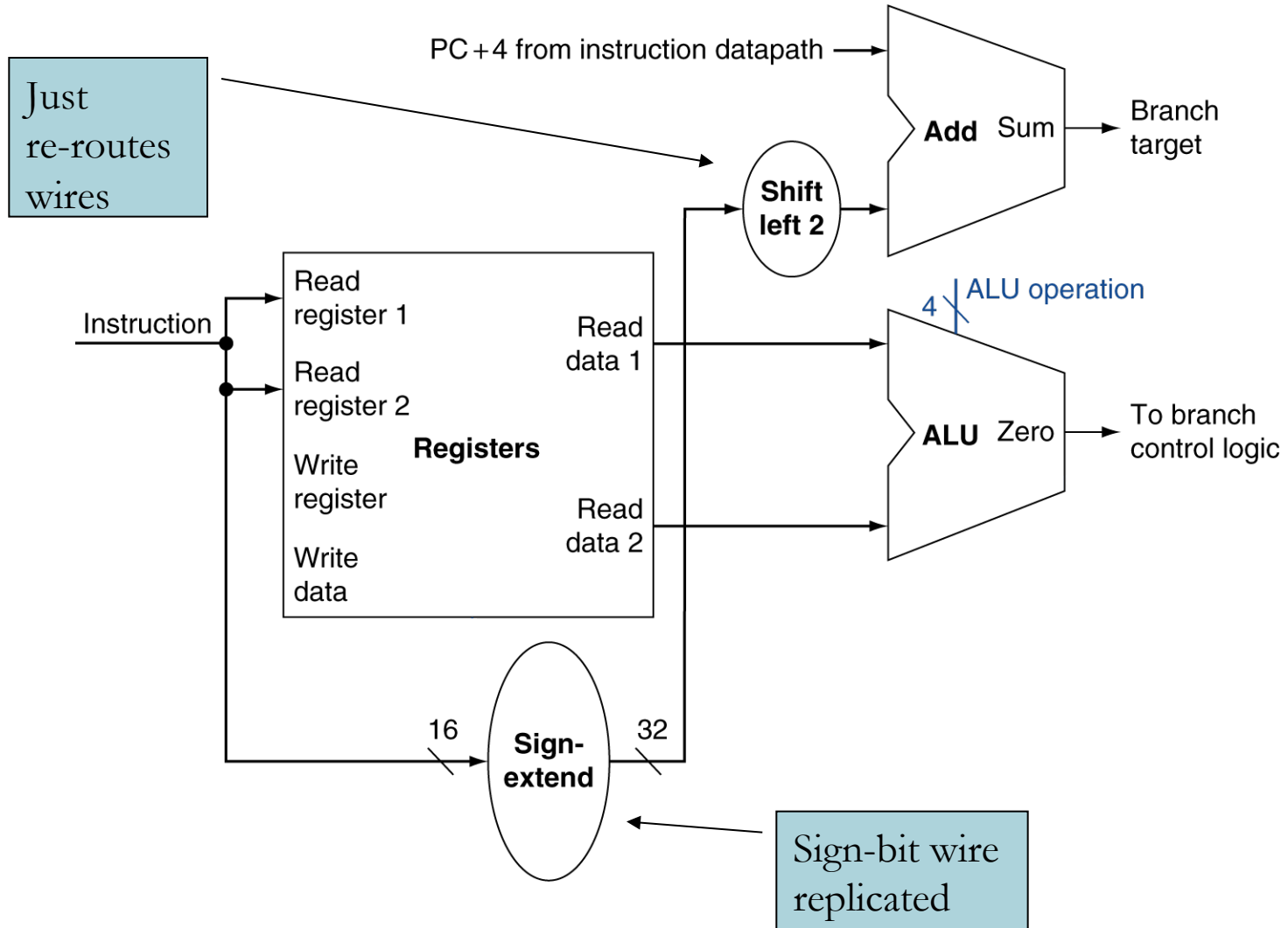


# Simplified Datapath

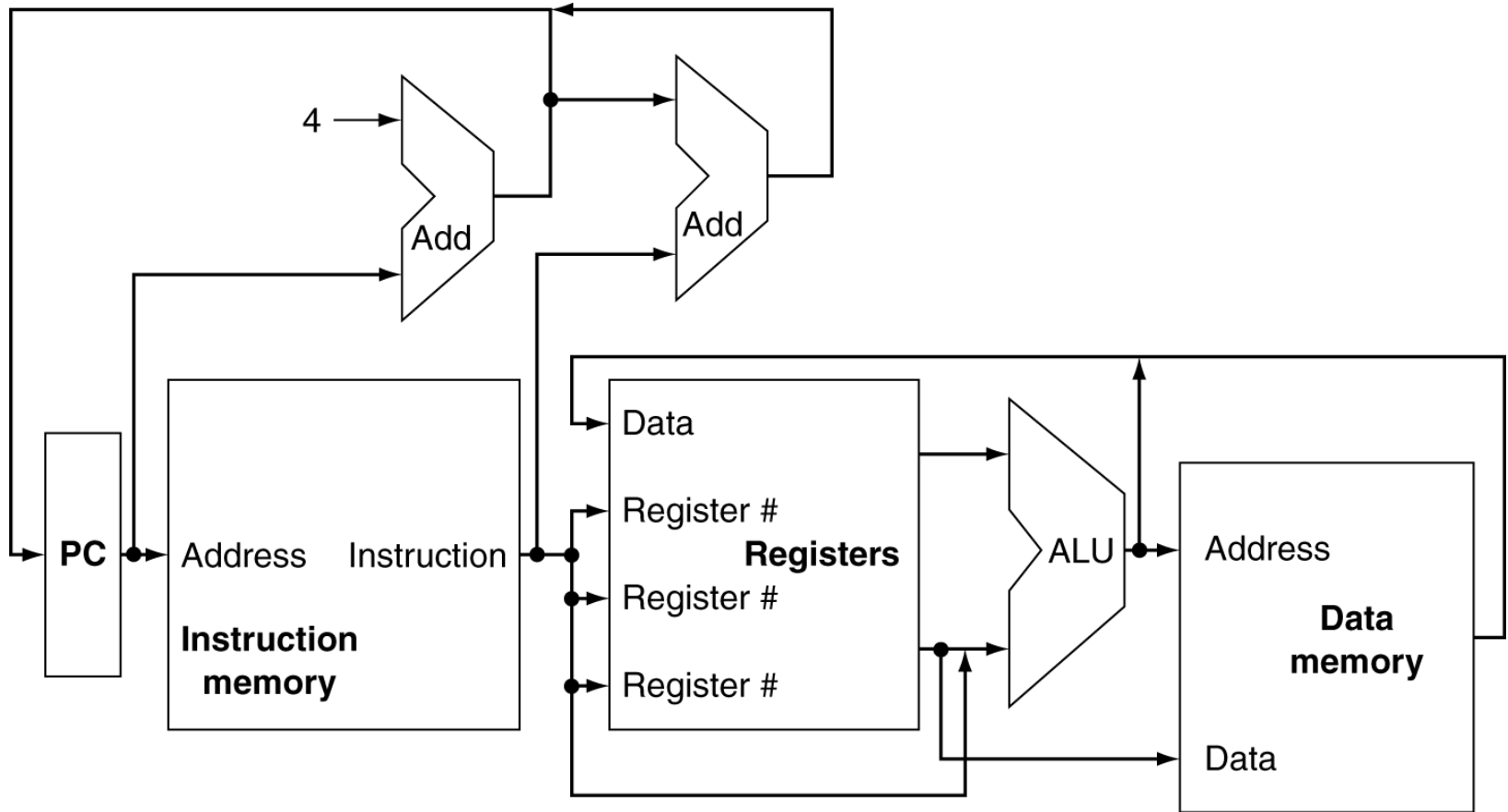


# Simplified Datapath

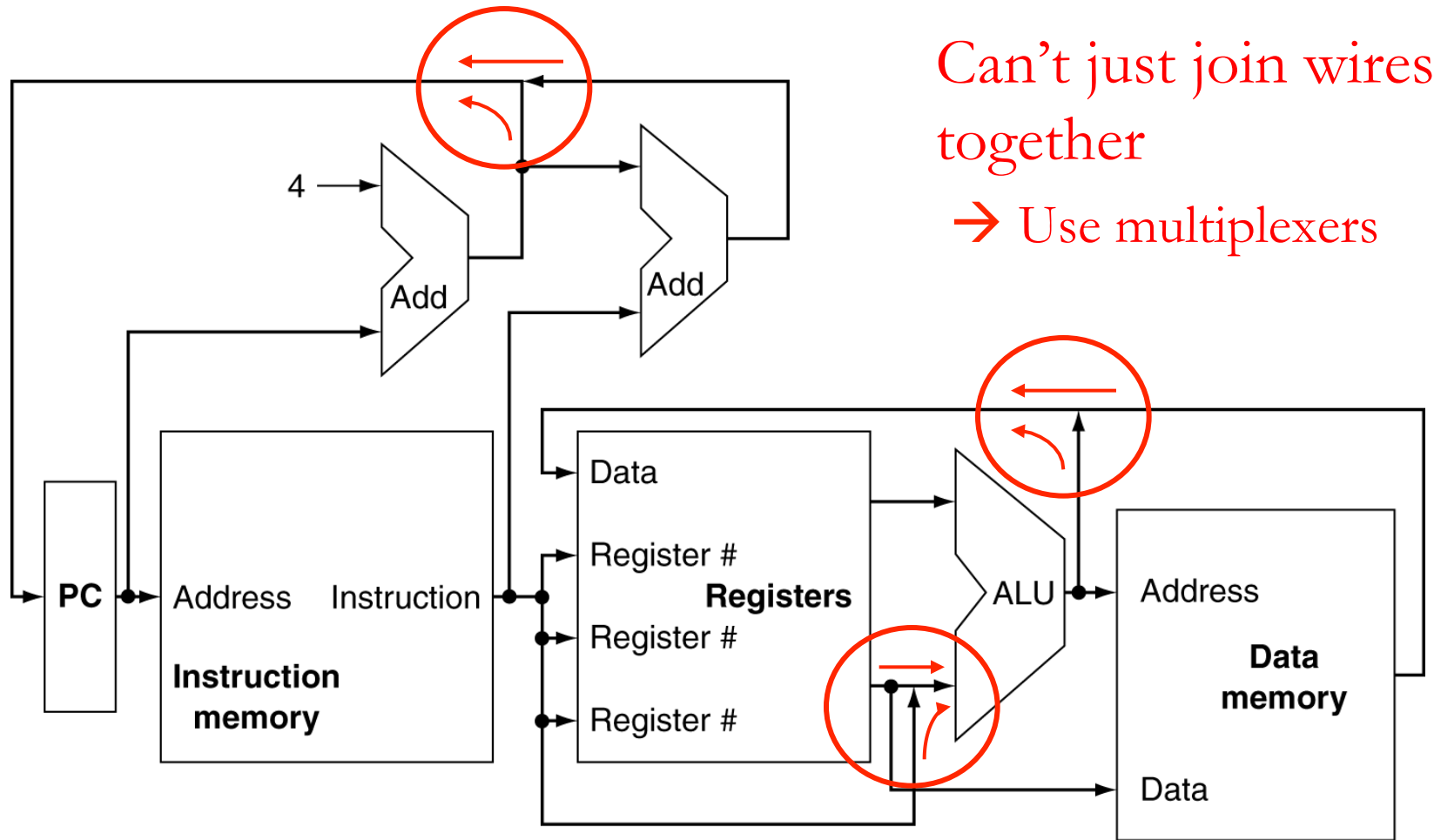


# Full Datapath

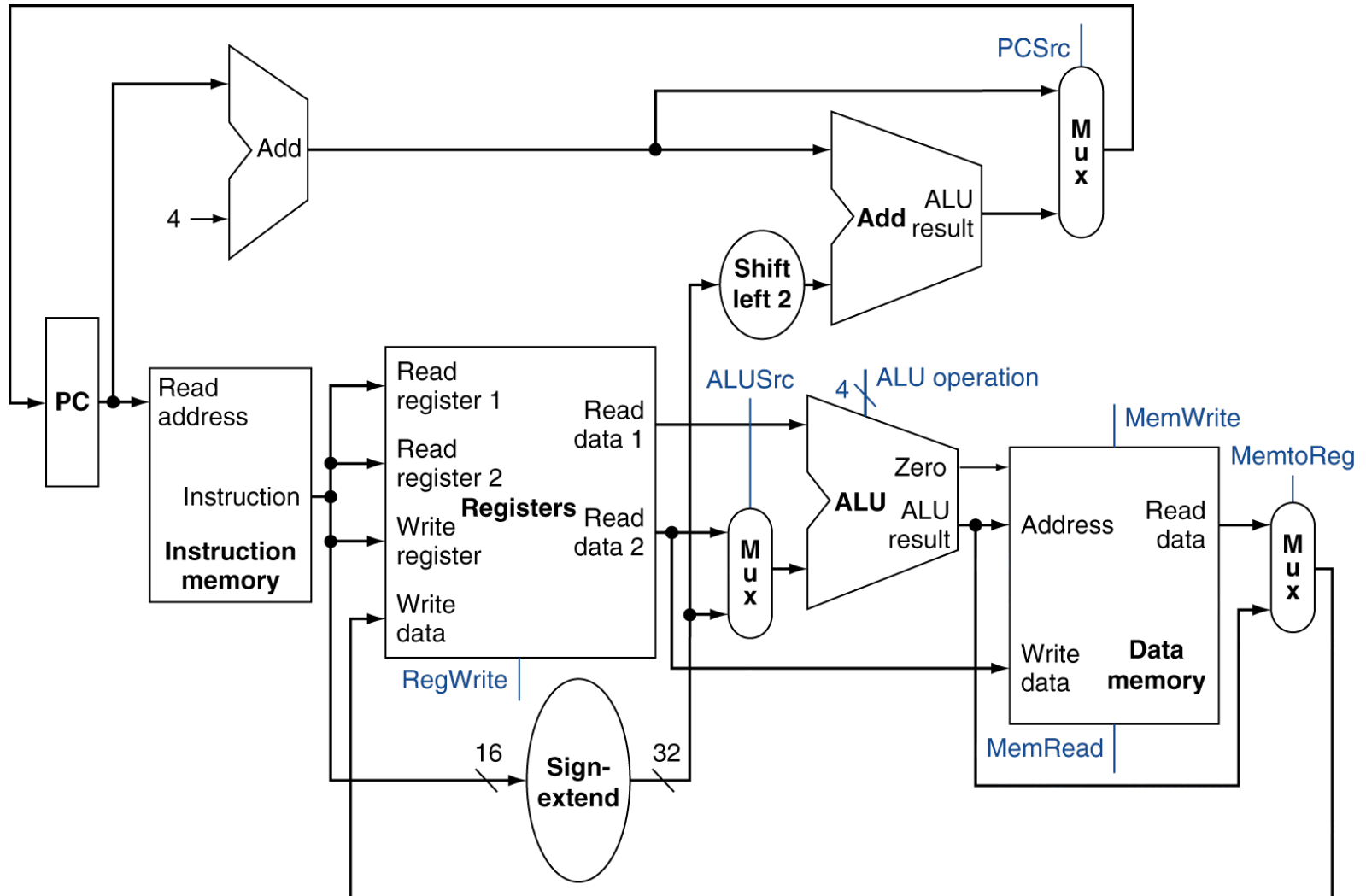


# Full Datapath

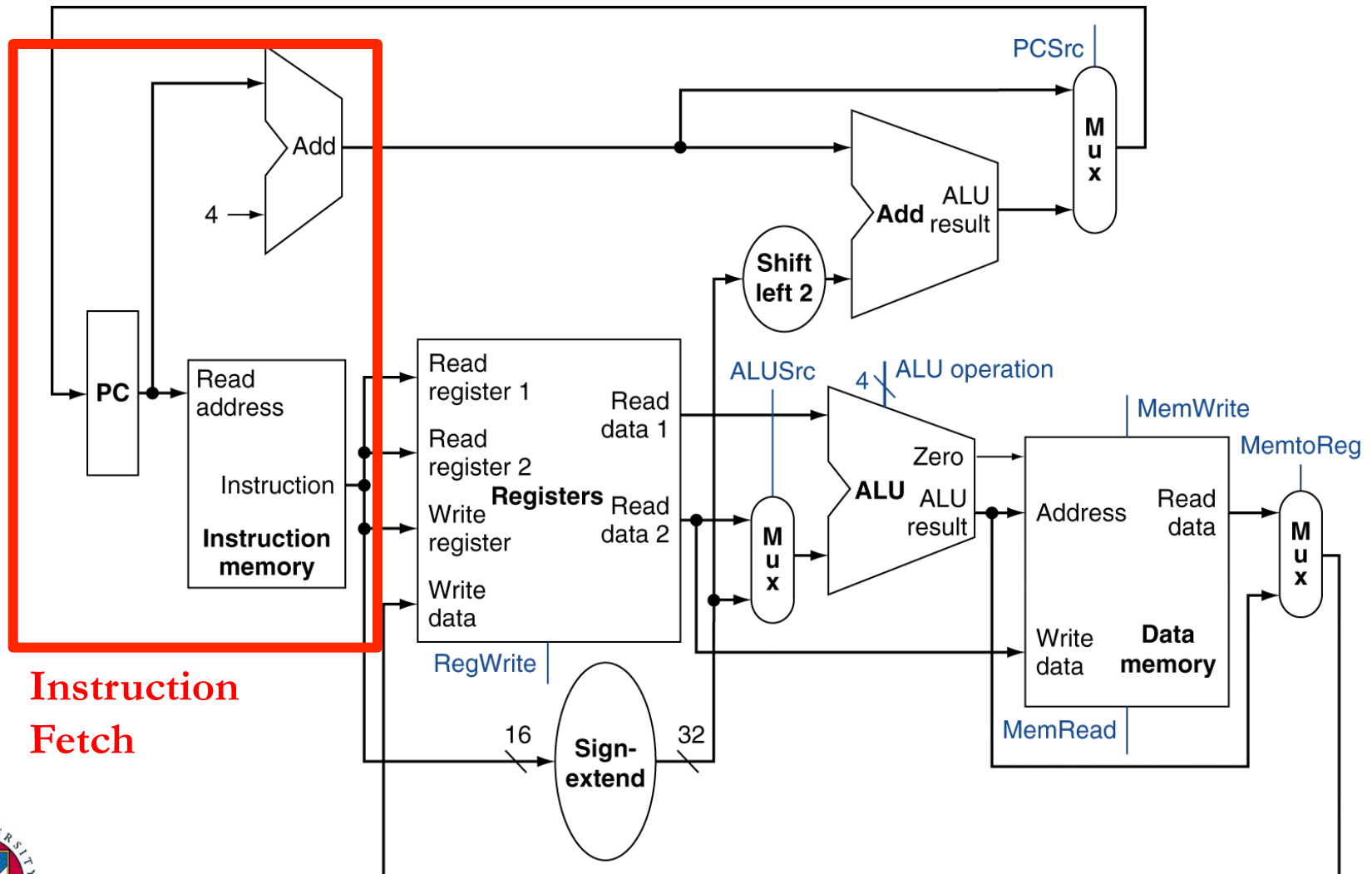

# Full Datapath

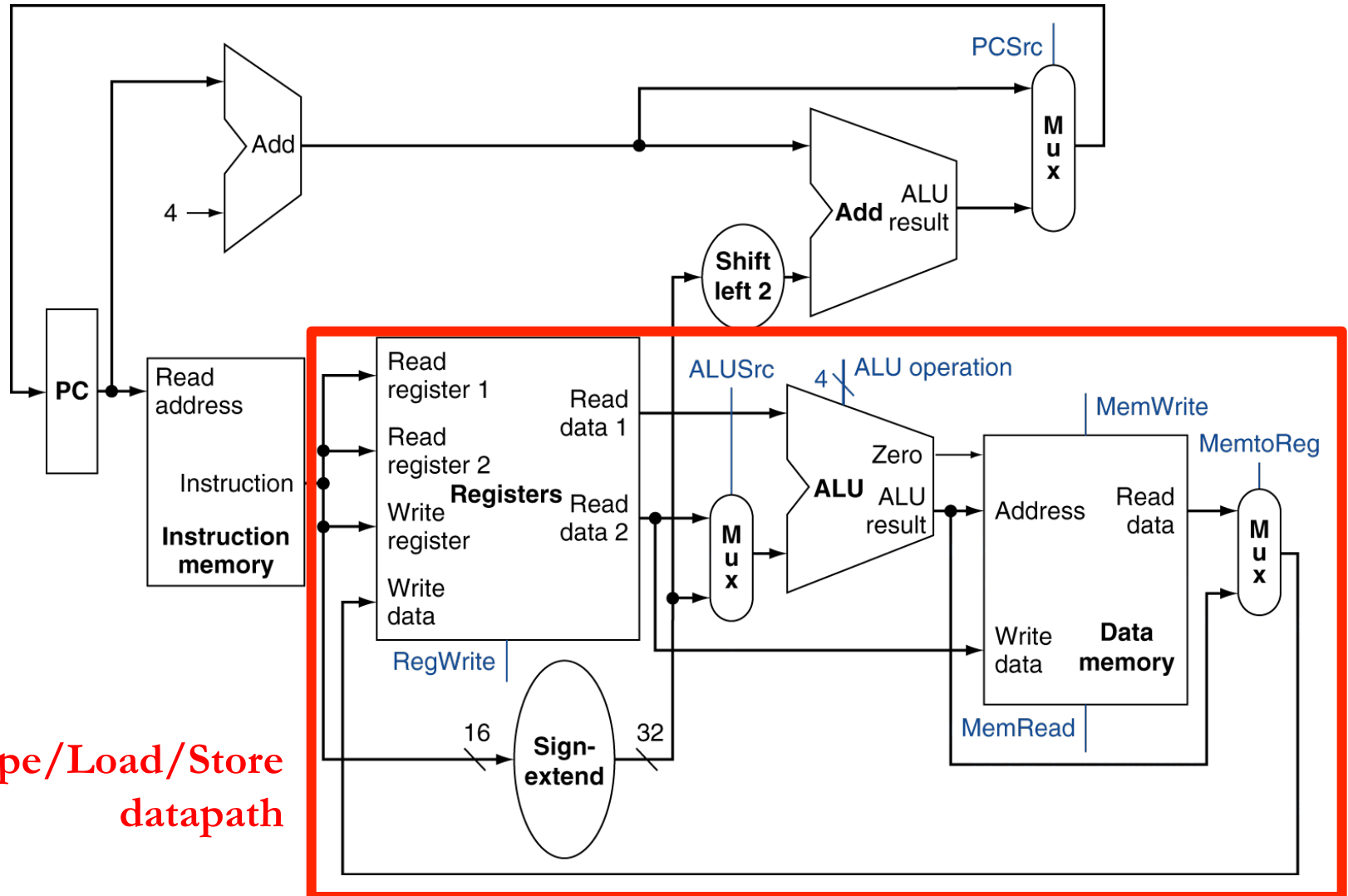

# Full Datapath

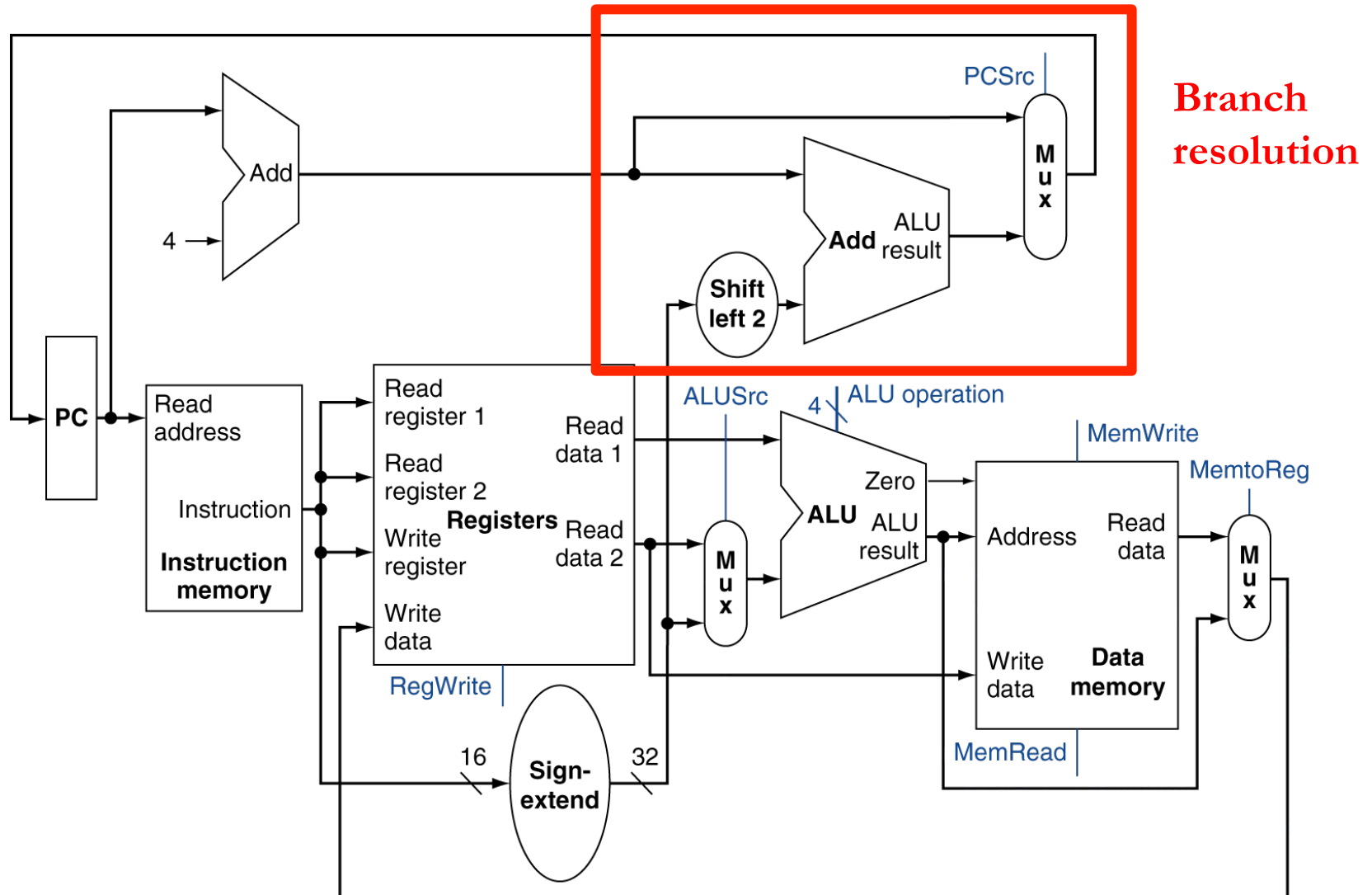




# How to design the control part

---


- For all control signals determine which value selects what operation, input, etc.
- Make truth table of control signal values for each instruction, or instruction group
- Convert table to combinational circuit
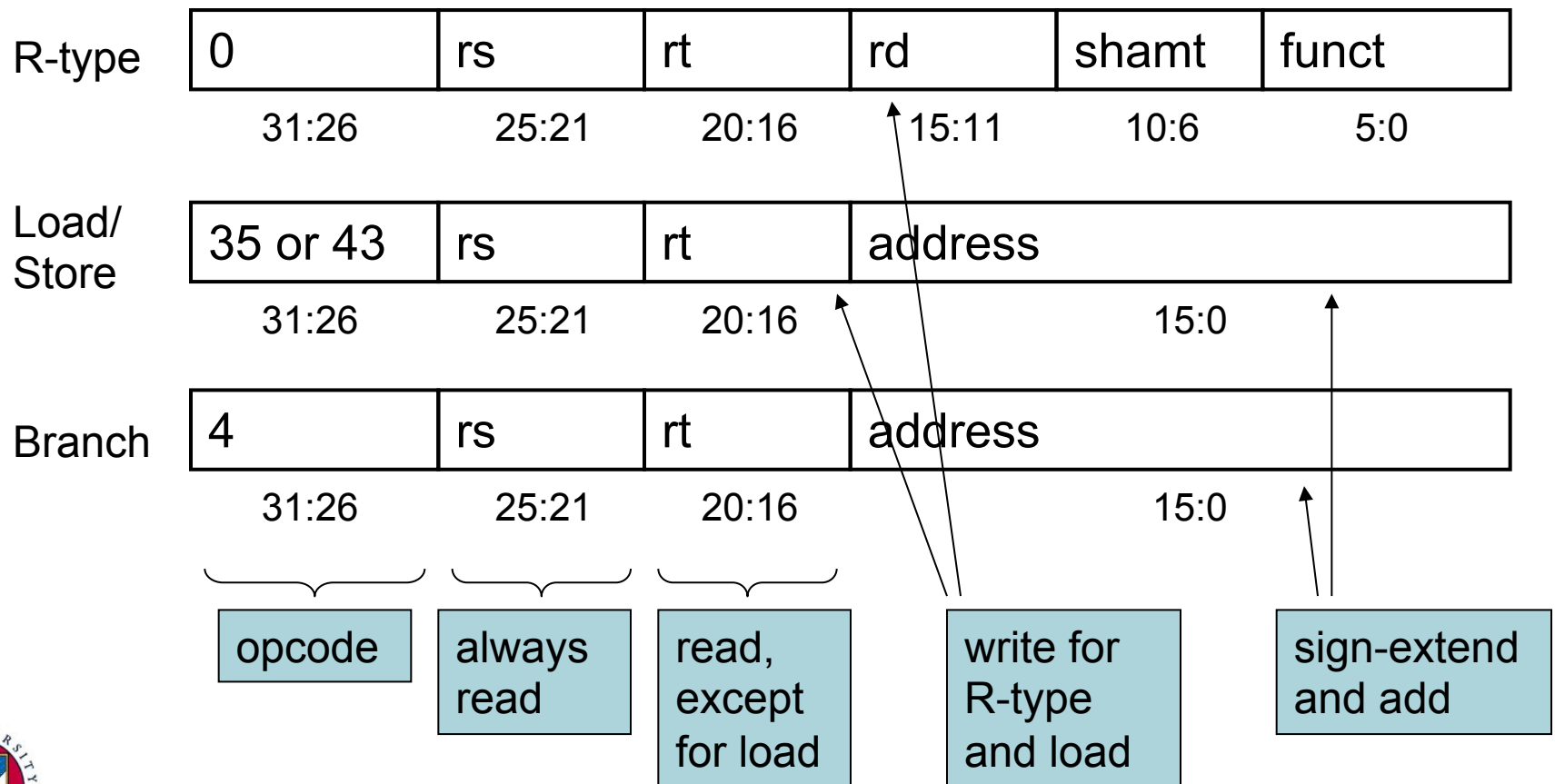
# Designing the Main Control Unit


Control signals derived from instruction fields



# Datapath with Control

 

# Datapath and control truth table

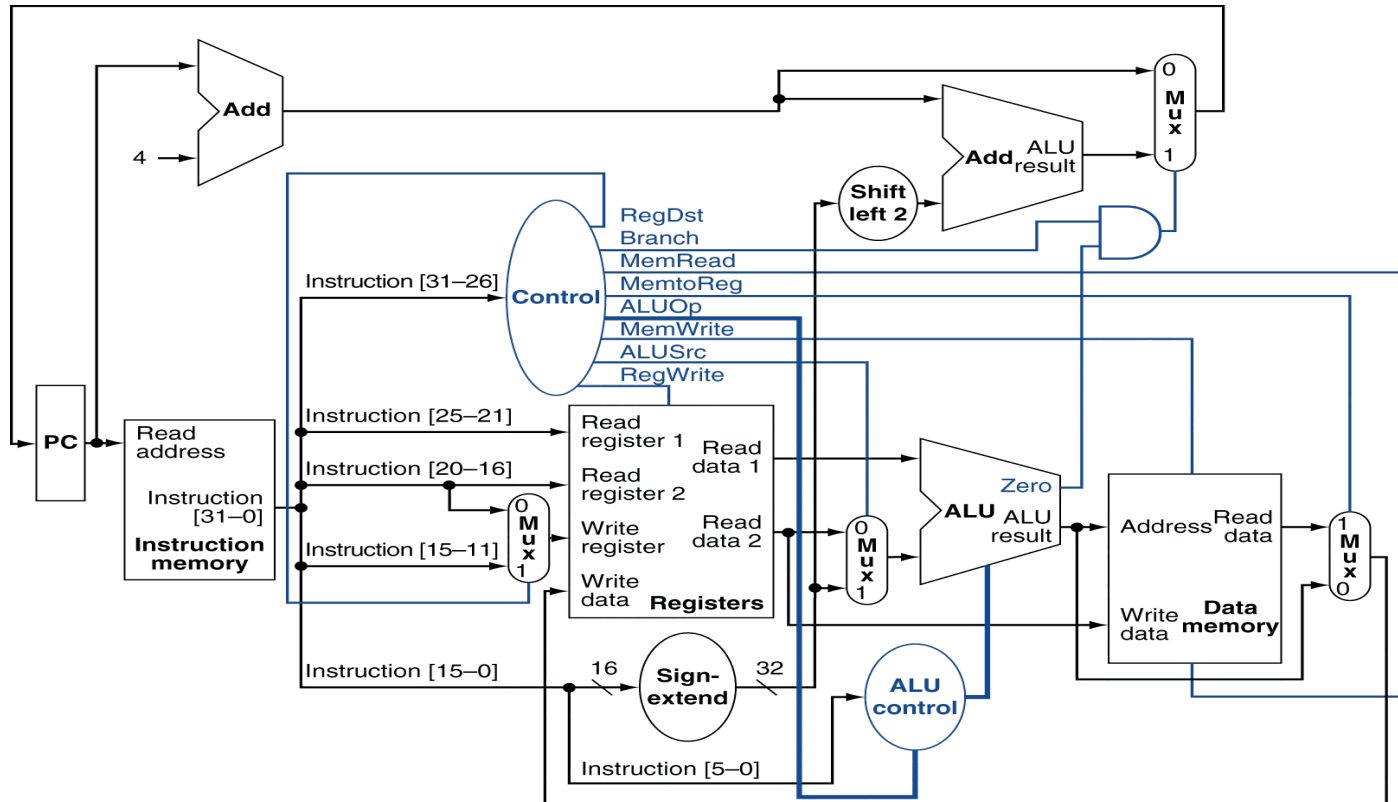

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1




**Don't Care**

# ALU control
 
## ALU operation:

- Data transfers (ld/st) – add
  - Branches – sub
  - All other – determined by funct field, I[5:0]
- derived from opcode



# ALU control

---


ALU control is **hierarchical**:

- Main control specifies which of the 3 op types
  - Add, Sub, or based on Funct bits
- Second level provides actual ALU control signal


ALU operation	
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less than

} actual  
**ALU Control**  
signals

# R-type instruction execution

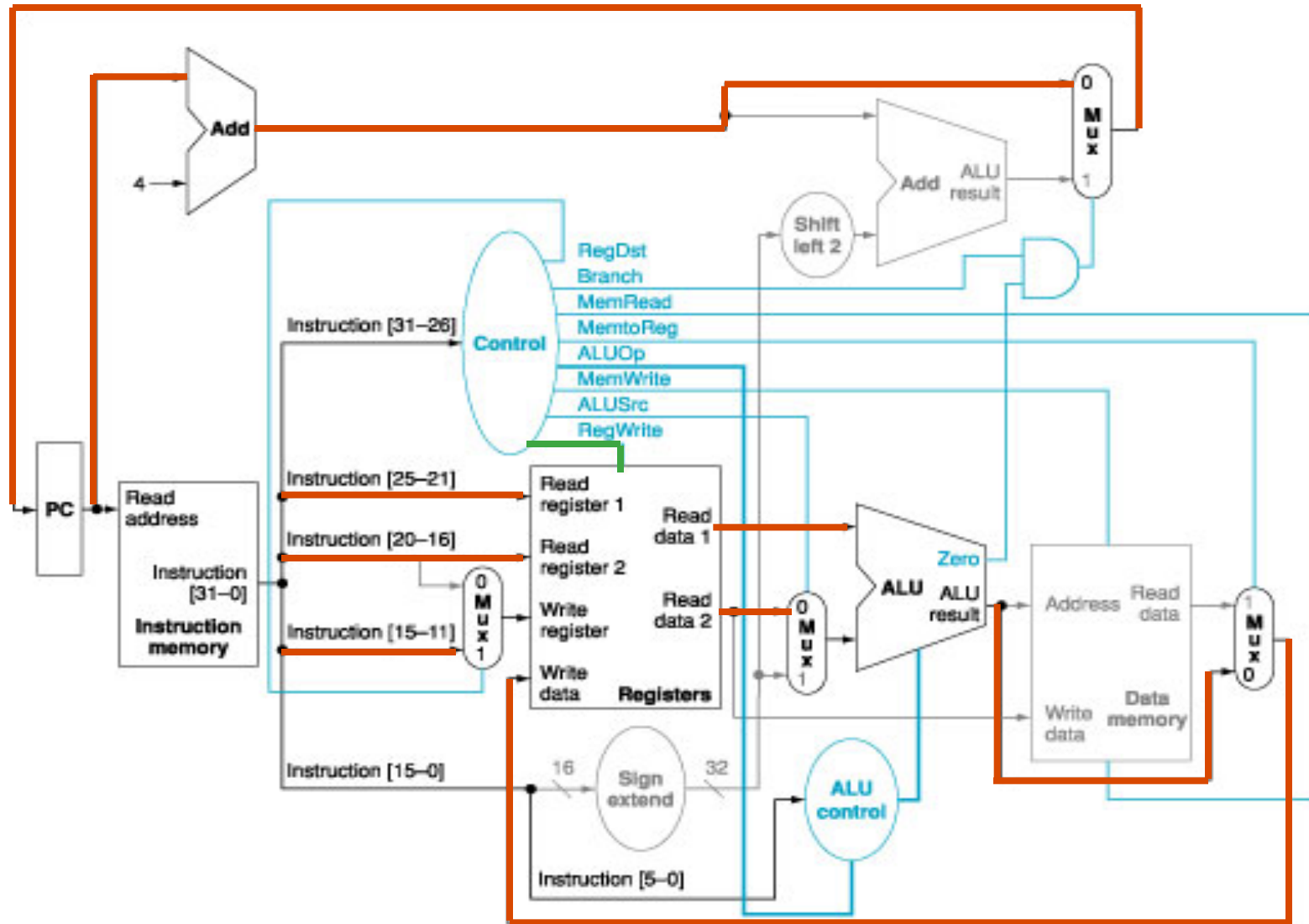


# lw execution

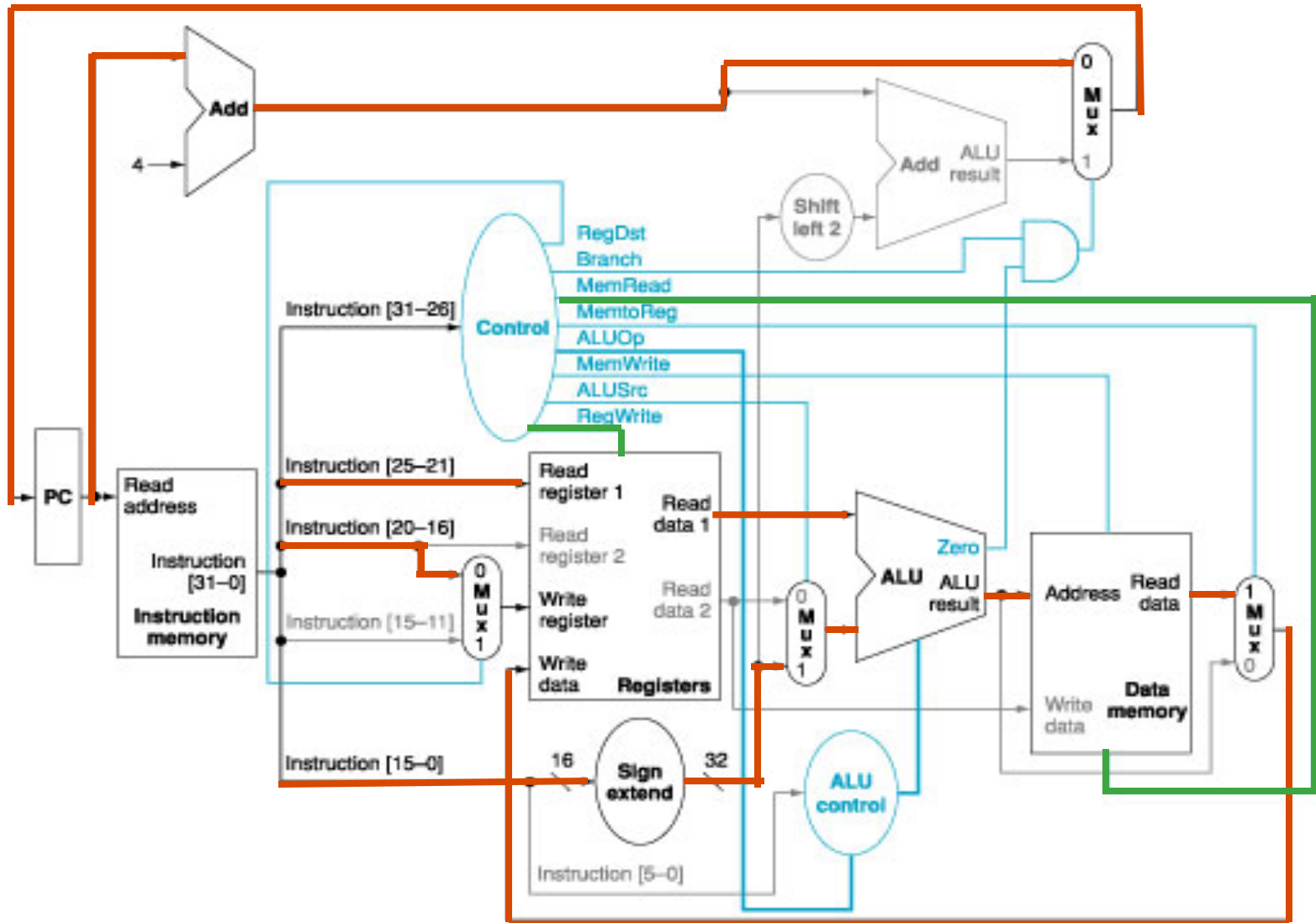





# beq (taken) execution

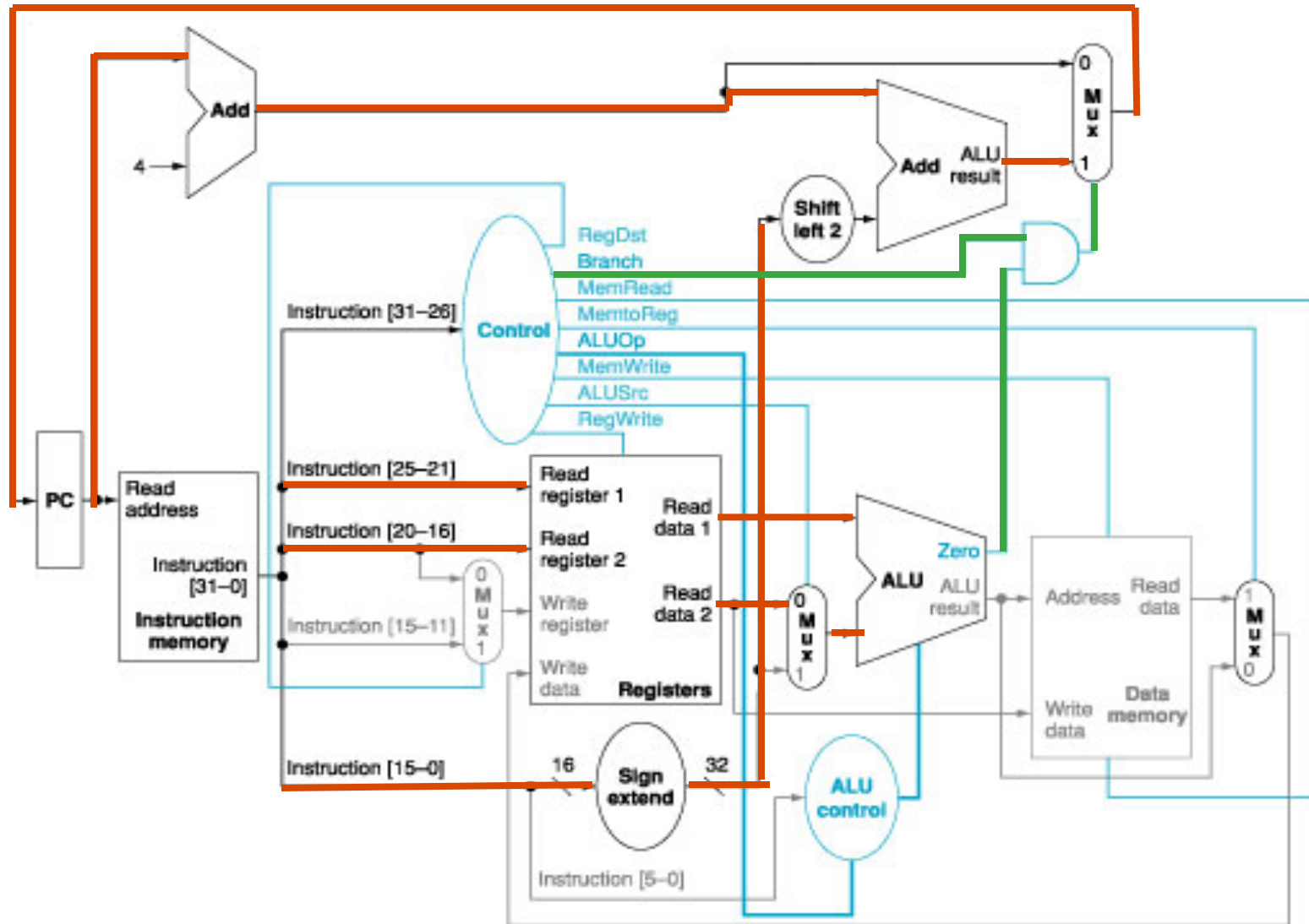
  
# Don't fall behind!

---

- Read the textbook (Chapter 4 in 4/e & 5/e)



- Multi-cycle datapath (Tues): on [Learn](#)
- Tutorials next week
  - Read the “multi-cycle datapath” chapter (on Learn) ahead of time if your section is Mon or Tues